

HW3

Mingxi Chen 999019482

Nr.1

State encoding:

FSM for X:

s_i : state in which A has been 1 for i cycles, if the next states make $X = 1$ (4 1 in total occurs, reset to s0)
(Y =0 if not be shown on the arc)

	s0	s1	s2	s3
S0	0	0	0	0
S1	0	0	1	1
S2	0	1	0	1



FSM for Y:

s_i : state in which A has been 1 consecitvely for i cycles. (3 1 consecitvely occurs, reset to s0)

	s0	s1	s2
S0	0	0	0
S1	0	0	1
S2	0	1	0

State transition diagram:

X, Y=0 if it's omitted on the arc.

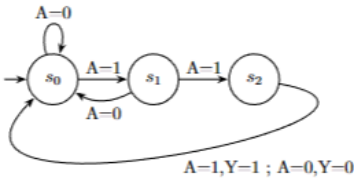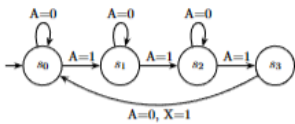

State tranision table:

FSM for X:

X	S[0:1]	A	s`	S`[0:1]
0	00	0	s0	00
0		1	s1	01
0	01	0	s1	01
0		1	s2	10
0	10	0	s2	10
0		1	s3	11
0	11	0	s3	11
1		1	s0	00

$$S'_0 = \bar{S}_0 S_1 A + S_0 \bar{S}_1 + S_0 S_1 \bar{A}$$
$$S'_1 = \bar{S}_0 \bar{S}_1 A + \bar{S}_0 S_1 \bar{A} + S_0 \bar{S}_1 A + S_0 S_1 \bar{A}$$

$$X = S_0S_1A$$

FSM for Y:


Y	S[0:1]	A	s`	S`[0:1]
0	00	0	s0	00
0		1	s1	01
0	01	0	s0	00
0		1	s2	10
1	10	0	s0	00
0		1	s0	00

$$S'_0 = \bar{S}_0S_1A$$

$$S'_1 = \bar{S}_0\bar{S}_1A$$

$$Y = S_0\bar{S}_1\bar{A}$$

schematic

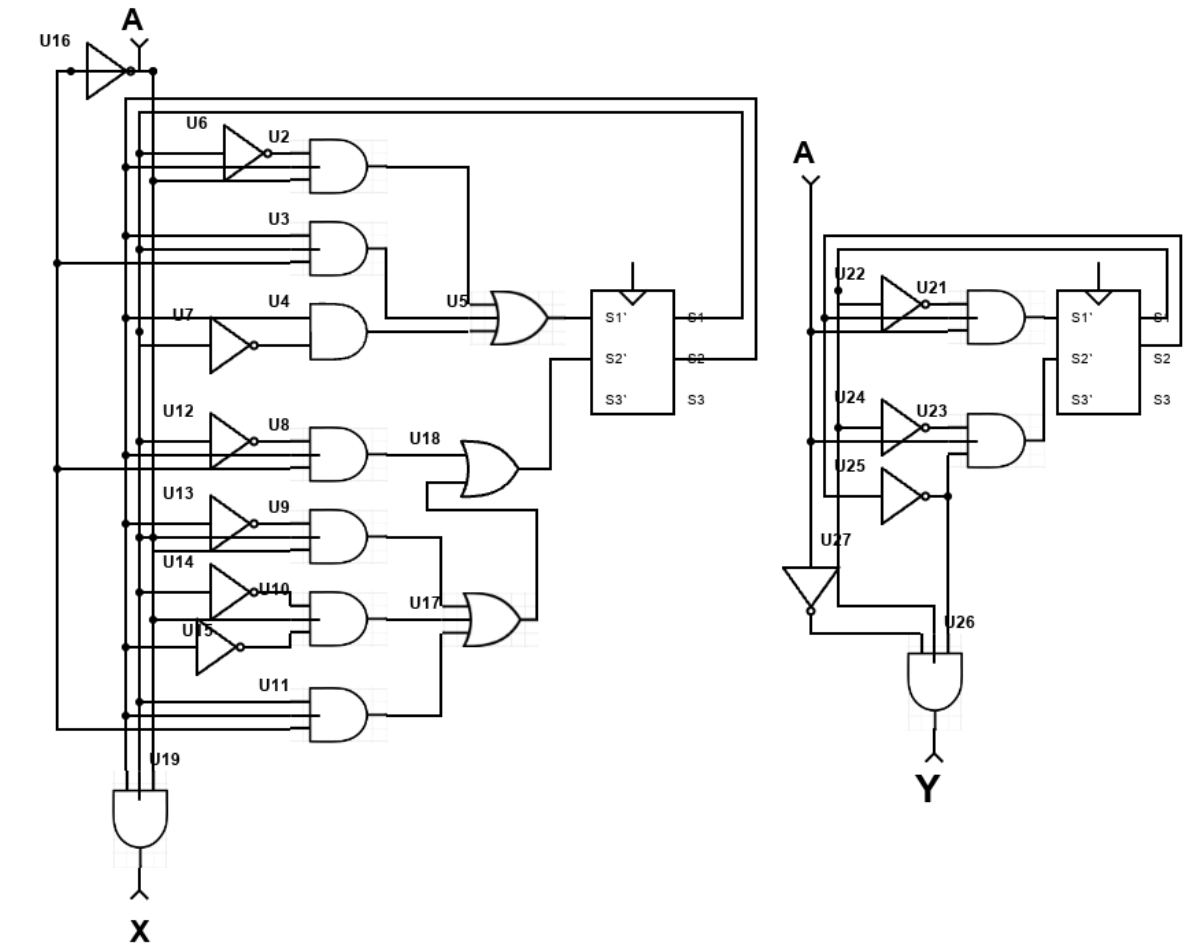

Nr.2

States encoding:

s_0 : pattern 0 occurs

s_1 : pattern 01 occurs

s_2 : pattern 010 occurs

s_3 : pattern 0100 or 0111 occurs

s_4 : pattern 011 occurs

s_5 : pattern 1 occurs

A: input


X: output

We consider the FST for pattern recognition task is cyclic(for asylic situation just ending in the s_3).

	s0	s1	s2	s3	s4	s5
S0	0	0	0	0	1	1
S1	0	0	1	1	0	0
S2	0	1	0	1	0	1

States transition diagram:

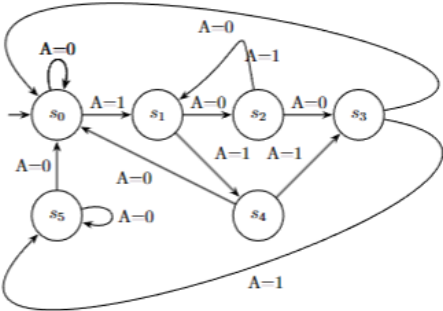Initial state can be s_0 or s_5
Only output 1 when s_3 is reached, then reset.(for acyclic siutation, end here)



States transition table:

X	s	S[2:0]	S`[2:0]	s`	A
0	s0	000	001	s1	0
0			000	s0	1
0	s1	001	010	s2	0
0			100	s4	1
1	s2	010	011	s3	0
0			001	s1	1
0	s3	011	000	s0	0
0			101	s5	1
0	s4	100	000	s0	0
1			011	s3	1
0	s5	101	000	s0	0
0			101	s5	1

Next state:

$S_0 = \overline{S_0} \overline{S_1} \overline{S_2} A + \overline{S_0} S_1 \overline{S_2} + S_0 S_1 \overline{S_2} A + \overline{S_1} S_2 A$
 $S_1 = S_0 \overline{S_1} \overline{S_2} \overline{A} + \overline{S_0} S_1 \overline{S_2} \overline{A}$
 $S_2 = S_0 \overline{S_1} \overline{S_2} A + S_0 S_1 \overline{S_2} A + S_0 \overline{S_1} S_2 A$

Output:

$X = \overline{S_0} \overline{S_1} \overline{S_2} A + \overline{S_0} \overline{S_1} S_2 A$

Nr.3


This is usually considered as a mealy machine, in which the output depend both on inputs and current states. But taking input as part of states makes it a moore machine.

States encoding:

$s_0 : A_{n-1} = 0$
 $s_1 : A_{n-1} = 1$
 $s_0 : S = 0, s_1 : S = 1$

States transition diagram:

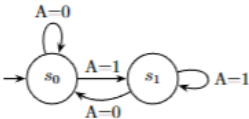Notice that A_{n-1} is equivalent to S
Ouput $Z = S \overline{B} + S A B$, which is not shown in graph because it's just *combinatoric_func(S, A, B)*



States transition table:


S	Bn	An(S`)	Zn
0	0	0 1	0 0
0	1	0 1	0 0
1	0	0 1	1 1
1	1	0 1	0 1

Next states and output:

$$S' = A_n$$

$$Z_n = A_{n-1}\bar{B}_n + A_{n-1}A_nB_n$$

Schematic:

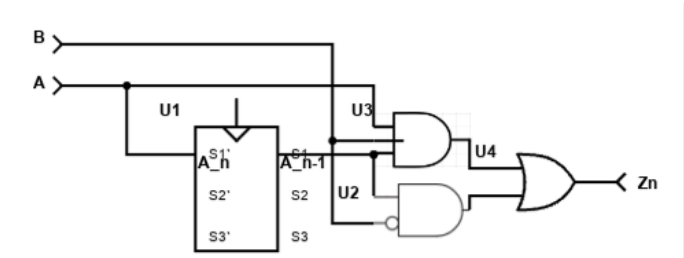

Nr.4

Prove that any Moore machine can be transformed into an equivalent Mealy machine:

For Moore machine, $\exists f : s_i \rightarrow Y$, we can easily associate a boolean function and input x such that $bool(s_i, x) = f(s_i)$, the new relation of output with x and s_i implies it's a mealy machine now.

Prove that any Mealy machine can be transformed into an equivalent Moore machine:

We again use a construction to prove any mealy machine can be transformed.

$\forall s_i, x_i, f(x_i, s_i)$ where x_i is input ,f()is output, we define new states:

$$s'_i = s_i x_i, s''_i = s_i \bar{x}_i.$$

$$\text{Let } f'(s'_i) = f(s_i, x_i), f''(s''_i) = f(s_i, \bar{x}_i)$$

Now we get a moore machine with the same evaluation of the mealy machine.

Program explanation:

see the `main.py` which implement the functionality specified in the assignment.

Notice:

The count of minterms in s_i is count of 1 in it. Because the min-terms are those $bool_{s_k}$ such that $S_0(i, j) = 1$

Usage:

```
# change the fsm matrix in main.py
fsm = [ [1,1,1],
        [0,0,0],
        [2,2,2]]

python main.py
```

Test:

```
python main.py
```

The input matrix is:
[2, 3, 1, 0]
[1, 3, 2, 1]
[2, 3, 3, 1]
[3, 3, 3, 3]

The s0 matrix is:
[0, 1, 1, 0]
[1, 1, 0, 1]
[0, 1, 1, 1]
[1, 1, 1, 1]
The count of min-terms in s0 is 12

The s1 matrix is:
[1, 1, 0, 0]
[0, 1, 1, 0]
[1, 1, 1, 0]
[1, 1, 1, 1]
The count of min-terms in s1 is 11